

ELEC 374 CPU Design – Phase 2

David-Alexandre Edwards (20099471),

Elan Bibas (20099396),

Hannah Berthiaume (20114482)

Verilog Code

DataPath

```
//added write signal to DataPath
module DataPath(
    input PCout, Zlowout, MDROUT, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Write
    ,
    input [4:0] aluControl,
    input clock, clear,
    input Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn, HIout, incPC
);

//registers run behavior every positive clock edge, bus will update BusMuxOUT whe
n a change in register output is detected
//define signals that will connect regiters to bus
wire [31:0] BusMuxOut;
wire [31:0] BusMuxInR0;
wire [31:0] BusMuxInR1;
wire [31:0] BusMuxInR2;
wire [31:0] BusMuxInR3;
wire [31:0] BusMuxInR4;
wire [31:0] BusMuxInR5;
wire [31:0] BusMuxInR6;
wire [31:0] BusMuxInR7;
wire [31:0] BusMuxInR8;
wire [31:0] BusMuxInR9;
wire [31:0] BusMuxInR10;
wire [31:0] BusMuxInR11;
wire [31:0] BusMuxInR12;
wire [31:0] BusMuxInR13;
wire [31:0] BusMuxInR14;
wire [31:0] BusMuxInR15;
wire [31:0] BusMuxInZHi;
wire [31:0] BusMuxInZLo;
wire [31:0] BusMuxInPC;
wire [31:0] BusMuxInMDR;
wire [31:0] BusMuxInRinP;
wire [31:0] BusMuxInCSign;
wire [31:0] BusMuxInRY;
wire [31:0] ALULoOut;
wire [31:0] ALUHiOut;
//phase 2
```

```

wire [8:0] Address;
wire [31:0] ramOut;
wire [31:0] BusMuxInIR;
wire r0out;
wire r1out;
wire R2out;
wire r3out;
wire R4out;
wire r5out;
wire r6out;
wire r7out;
wire r8out;
wire r9out;
wire r10out;
wire r11out;
wire r12out;
wire r13out;
wire r14out;
wire r15out;
wire [31:0] BusMuxInRoutP;
wire [31:0] BusMuxInRHi;
// phase 3
wire branch;

//instantiate all register
register R1(clock, clear, R1in, BusMuxOut, BusMuxInR1);
register R2(clock, clear, R2in, BusMuxOut, BusMuxInR2);
register R3(clock, clear, R3in, BusMuxOut, BusMuxInR3);
register R4(clock, clear, R4in, BusMuxOut, BusMuxInR4);
register R5(clock, clear, R5in, BusMuxOut, BusMuxInR5);
register R6(clock, clear, R6in, BusMuxOut, BusMuxInR6);
register R7(clock, clear, R7in, BusMuxOut, BusMuxInR7);
register R8(clock, clear, R8in, BusMuxOut, BusMuxInR8);
register R9(clock, clear, R9in, BusMuxOut, BusMuxInR9);
register R10(clock, clear, R10in, BusMuxOut, BusMuxInR10);
register R11(clock, clear, R11in, BusMuxOut, BusMuxInR11);
register R12(clock, clear, R12in, BusMuxOut, BusMuxInR12);
register R13(clock, clear, R13in, BusMuxOut, BusMuxInR13);
register R14(clock, clear, R14in, BusMuxOut, BusMuxInR14);
register R15(clock, clear, R15in, BusMuxOut, BusMuxInR15);
register RHi(clock, clear, RHiIn, BusMuxOut, BusMuxInRHi);
register RLO(clock, clear, RLOIn, BusMuxOut, BusMuxInRLo);
register RZHi(clock, clear, Zin, ALUHiOut, BusMuxInZHi);
register RZLO(clock, clear, Zin, ALULoOut, BusMuxInZLo);
//register PC(clock, clear, PCIn, BusMuxOut, BusMuxInPC);

```

```

register RInP(clock, clear, RInPin, BusMuxOut, BusMuxInRInP);
//register RCSign(clock, clear, RCSignIn, BusMuxOut, BusMuxInCSign);
register RoutP(clock, clear, RoutPin, BusMuxOut, BusMuxInRoutP);
register RY(clock, clear, Yin, BusMuxOut, BusMuxInRY);

//phase 2 Select and Encode
SelectEncode selectencode(BusMuxInIR, Gra, Grb, Grc, Rin, Rout, BAout, BusMuxInC
Sign, R0in, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R
12in, R13in, R14in, R15in, R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out
, R8out, R9out, R10out, R11out, R12out, R13out, R14out, R15out);

//phase 2 Memory subsystem
register IR(clock, clear, IRin, BusMuxOut, BusMuxInIR);
register R0 R0(clock, clear, R0in, BAout, BusMuxOut, BusMuxInR0);
MAR mar(clock, clear, MARin, BusMuxOut, Address);
ram1 ram(Address, clock, BusMuxInMDR, Write, ramOut);
MDR mdr(clock, clear, MDRin, Read, BusMuxOut, ramOut, BusMuxInMDR);
pc PC(clock, clear, PCin, incPC, branch, BusMuxOut, BusMuxInPC); //incPC to PCin
to '1

//phase 2 conff
conff CONFF(BusMuxOut, BusMuxInIR, ConIn, branch);

//instantiate bus
bus cpuBUS(
    BusMuxInR0, BusMuxInR1, BusMuxInR2, BusMuxInR3, BusMuxInR4, BusMuxInR5, BusMuxInR6
, BusMuxInR7, BusMuxInR8, BusMuxInR9, BusMuxInR10, BusMuxInR11, BusMuxInR12, BusMuxInR13
, BusMuxInR14, BusMuxInR15,
    BusMuxInRHi, BusMuxInLo, BusMuxInZHi, BusMuxInZLo, BusMuxInPC, BusMuxInMDR, BusMuxI
nRInP, BusMuxInCSign,
    R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out, R11out, R12
out, R13out, R14out, R15out,
    HIout, LOout, Zhighout, Zlowout, PCout, MDRout, INportout, Cout, BusMuxOut
);

ALU alu(aluControl, BusMuxInRY, BusMuxOut, ALULoOut, ALUHiOut);

endmodule

//we essentially need to perform an action anytime one of the control signals cha
nges

```

```

// testbench changes state every rising-
// edge of clock, does the job associated with state for each
// #10 = time delay of 10 before instruction is ran, same concept with #15
// wires are used to create connection between to ports (input and output port),
// they do not store data, only drive data
// MDRout = 1, updates BusMuxOut with value of BusMuxInMDR, since R2in =1, R2 will
// hold value (write to register)
// the always @ block is used for cyclic behavior

```

Select & Encode

```

module SelectEncode(
    input [31:0] IR,
    input Gra, Grb, Grc, Rin, Rout, BAout,
    output [31:0] C_sign,
    output R0in, R1in, R2in, R3in, R4in, R5in, R6in, R7in, R8in, R9in, R10in, R11in, R12in,
    R13in, R14in, R15in,
    output R0out, R1out, R2out, R3out, R4out, R5out, R6out, R7out, R8out, R9out, R10out,
    R11out, R12out, R13out, R14out, R15out
);

```

```

//have two outputs instead
reg [3:0] OpCode, Ra, Rb, Rc;
reg [3:0] DecoderInput;
reg [15:0] DecoderOutput;
reg [15:0] Out;
reg [31:0] C_sign_extended;
reg [15:0] In;
reg temp;
integer i;

```

```

always @ (*) begin
    // Gra or Grb or Grc
    OpCode = IR[31:27];
    Ra = IR[26:23];
    Rb = IR[22:19];
    Rc = IR[18:15];

    if(Gra == 1) begin //Add
        DecoderInput = Ra;
    end
    else if(Grb == 1) begin //Sub

```

```

    DecoderInput = Rb;
end
else if(Grc == 1) begin //Shift Right
    DecoderInput = Rc;
end

if(DecoderInput == 4'b0000) begin
    DecoderOutput = 16'b0000000000000001;
end
else if(DecoderInput == 4'b0001) begin
    DecoderOutput = 16'b0000000000000010;
end
else if(DecoderInput == 4'b0010) begin
    DecoderOutput = 16'b0000000000000100;
end
else if(DecoderInput == 4'b0011) begin
    DecoderOutput = 16'b0000000000001000;
end
else if(DecoderInput == 4'b0100) begin
    DecoderOutput = 16'b0000000000010000;
end
else if(DecoderInput == 4'b0101) begin
    DecoderOutput = 16'b0000000000100000;
end
else if(DecoderInput == 4'b0110) begin
    DecoderOutput = 16'b0000000001000000;
end
else if(DecoderInput == 4'b0111) begin
    DecoderOutput = 16'b0000000010000000;
end
else if(DecoderInput == 4'b1000) begin
    DecoderOutput = 16'b0000000100000000;
end
else if(DecoderInput == 4'b1001) begin
    DecoderOutput = 16'b0000001000000000;
end
else if(DecoderInput == 4'b1010) begin
    DecoderOutput = 16'b0000010000000000;
end
else if(DecoderInput == 4'b1011) begin
    DecoderOutput = 16'b0000100000000000;
end
else if(DecoderInput == 4'b1100) begin
    DecoderOutput = 16'b0001000000000000;
end

```

```

else if(DecoderInput == 4'b1101) begin
    DecoderOutput = 16'b0010000000000000;
end
else if(DecoderInput == 4'b1110) begin
    DecoderOutput = 16'b0100000000000000;
end
else if(DecoderInput == 4'b1111) begin
    DecoderOutput = 16'b1000000000000000;
end
else begin
    DecoderOutput = 16'b0000000000000000;
end
for (i = 0 ; i < 16 ; i = i + 1)
    In[i] = DecoderOutput[i] & Rin;
temp = Rout | BAout;
for (i = 0 ; i < 16 ; i = i + 1)
    Out[i] = DecoderOutput[i] & temp;
C_sign_extended = {{13{IR[18]}}, {IR[18:0]}};

end
assign {R15in, R14in, R13in, R12in, R11in, R10in, R9in, R8in, R7in, R6in, R5in, R4in, R3in,
R2in, R1in, R0in} = In;
assign {R15out, R14out, R13out, R12out, R11out, R10out, R9out, R8out, R7out, R6out, R5out,
R4out, R3out, R2out, R1out, R0out} = Out;
assign C_sign = C_sign_extended;

endmodule

```

Conff

```

module conff(
    input [31:0] BusMuxIn,
    input [31:0] IR, // C2 = IR[22:19]
    input ConIn, // phase 3
    output branch
);

/*
make input BusMuxInIR 32 bits and isolate the 4 required bits
output name should be controlOut
you should have an always block that runs anytime inputs change
assign statement will need to be outside of always block (may need a temp reg variable and assign output to that outside always block)

*/

```

```

reg temp;
reg temp2;
reg [3:0] BusMuxInIR;
integer i;

always @ (ConIn) begin

    BusMuxInIR = IR[22:19];

    if (BusMuxInIR[0] == 1'b1) begin

        temp = BusMuxInIR[0] & ~(|BusMuxIn);    // IR[0] AND Bus
        // decoder[0] & (|bus)

        if (temp == 1'b1) begin                // if equals 0
            temp2 = 1'b1;
        end
    end
    else if (BusMuxInIR[1] == 1'b1) begin

        temp = BusMuxInIR[1] & (|BusMuxIn);    // IR[1] AND (NOT Bus)

        if (temp != 1'b0) begin                // if not equals 0
            // not working, c
            check with TA
            temp2 = temp;
        end
    end
    else if (BusMuxInIR[2] == 1'b1) begin
        temp = BusMuxInIR[2] & ~BusMuxIn[31];    // IR[2] AND (NOT Bus[31])
    end
    else if (BusMuxInIR[3] == 1'b1) begin
        temp = BusMuxInIR[3] & BusMuxIn[31];    // IR[3] AND Bus[31]
        // if less than 0
        after than equal to 0
        temp2 = temp;
    end
    else if (BusMuxInIR[3] == 1'b1) begin
        temp = BusMuxInIR[3] & BusMuxIn[31];    // IR[3] AND Bus[31]
        // if less than 0
        an 0
        temp2 = temp;
    end
end

```



```

    end

    if (ConIn == 1'b0) begin
        temp2 = 1'b0;
    end

end

assign branch = temp2; // (((temp[0] | temp[1]) | temp[2]) | temp[3]);

endmodule

```

MAR

```

module MAR(input clock, input clear, input MARin, input [31:0] BusMuxOut, output
[8:0] Address);

reg [31:0] q;
    // Behavioral section for writing to the register
    always @ ( posedge clock)
        begin
            if(clear) begin
                q <= 32'b0;
            end
            else if(MARin) begin
                q <= BusMuxOut;
            end
        end

    assign Address = q[8:0];

endmodule

```

MDR

```

module MDR(
    input clk, clear, MDRin, read,
    input [31:0] BusMuxOut,
    input [31:0] Mdatain,
    output [31:0] BusMuxInMDR
);

```

```

// Behavioral section for writing to the register
reg [31:0] Din;
reg [31:0] In;
always @ (posedge clk)
    begin
        if (read) begin
            Din <= Mdatain;
        end
        else begin
            Din <= BusMuxOut;
        end

        if(clear) begin
            In <= 32'b0;
        end
        else if(MDRin) begin
            In <= Din;
        end
    end

    assign BusMuxInMDR = In;

endmodule

```

RAM

```

// megafunction wizard: %RAM: 1-PORT%
// GENERATION: STANDARD
// VERSION: WM1.0
// MODULE: altsyncram

// =====
// File Name: ram1.v
// Megafunction Name(s):
//     altsyncram
//
// Simulation Library Files(s):
//     altera_mf
// =====
// *****
// THIS IS A WIZARD-GENERATED FILE. DO NOT EDIT THIS FILE!
//
// 13.0.1 Build 232 06/12/2013 SP 1 SJ Full Version
// *****

```

```
//Copyright (C) 1991-2013 Altera Corporation
//Your use of Altera Corporation's design tools, logic functions
//and other software and tools, and its AMPP partner logic
//functions, and any output files from any of the foregoing
//(including device programming or simulation files), and any
//associated documentation or information are expressly subject
//to the terms and conditions of the Altera Program License
//Subscription Agreement, Altera MegaCore Function License
//Agreement, or other applicable license agreement, including,
//without limitation, that your use is for the sole purpose of
//programming logic devices manufactured by Altera and sold by
//Altera or its authorized distributors. Please refer to the
//applicable agreement for further details.
```

```
// synopsys translate_off
`timescale 1 ps / 1 ps
// synopsys translate_on
module ram1 (
    address,
    clock,
    data,
    wren,
    q);

    input  [8:0]  address;
    input        clock;
    input  [31:0] data;
    input        wren;
    output [31:0] q;

    `ifndef ALTERA_RESERVED_QIS
// synopsys translate_off
`endif
        tri1        clock;
    `ifndef ALTERA_RESERVED_QIS
// synopsys translate_on
`endif

    wire [31:0] sub_wire0;
    wire [31:0] q = sub_wire0[31:0];

    altsyncram altsyncram_component (
        .address_a (address),
        .clock0 (clock),
        .data_a (data),
```

```

        .wren_a (wren),
        .q_a (sub_wire0),
        .aclr0 (1'b0),
        .aclr1 (1'b0),
        .address_b (1'b1),
        .addressstall_a (1'b0),
        .addressstall_b (1'b0),
        .byteena_a (1'b1),
        .byteena_b (1'b1),
        .clock1 (1'b1),
        .clocken0 (1'b1),
        .clocken1 (1'b1),
        .clocken2 (1'b1),
        .clocken3 (1'b1),
        .data_b (1'b1),
        .eccstatus (),
        .q_b (),
        .rden_a (1'b1),
        .rden_b (1'b1),
        .wren_b (1'b0));

defparam
    altsyncram_component.clock_enable_input_a = "BYPASS",
    altsyncram_component.clock_enable_output_a = "BYPASS",
`ifdef NO_PLI
    altsyncram_component.init_file = "lab.rif"
`else
    altsyncram_component.init_file = "lab.hex"
`endif
,

    altsyncram_component.intended_device_family = "Cyclone III",
    altsyncram_component.lpm_hint = "ENABLE_RUNTIME_MOD=NO",
    altsyncram_component.lpm_type = "altsyncram",
    altsyncram_component.numwords_a = 512,
    altsyncram_component.operation_mode = "SINGLE_PORT",
    altsyncram_component.outdata_aclr_a = "NONE",
    altsyncram_component.outdata_reg_a = "UNREGISTERED",
    altsyncram_component.power_up_uninitialized = "FALSE",
    altsyncram_component.read_during_write_mode_port_a = "DONT_CARE",
    altsyncram_component.widthad_a = 9,
    altsyncram_component.width_a = 32,
    altsyncram_component.width_byteena_a = 1;

endmodule

```

```
// =====
// CNX file retrieval info
// =====
// Retrieval info: PRIVATE: ADDRESSSTALL_A NUMERIC "0"
// Retrieval info: PRIVATE: AclrAddr NUMERIC "0"
// Retrieval info: PRIVATE: AclrByte NUMERIC "0"
// Retrieval info: PRIVATE: AclrData NUMERIC "0"
// Retrieval info: PRIVATE: AclrOutput NUMERIC "0"
// Retrieval info: PRIVATE: BYTE_ENABLE NUMERIC "0"
// Retrieval info: PRIVATE: BYTE_SIZE NUMERIC "8"
// Retrieval info: PRIVATE: BlankMemory NUMERIC "0"
// Retrieval info: PRIVATE: CLOCK_ENABLE_INPUT_A NUMERIC "0"
// Retrieval info: PRIVATE: CLOCK_ENABLE_OUTPUT_A NUMERIC "0"
// Retrieval info: PRIVATE: Clken NUMERIC "0"
// Retrieval info: PRIVATE: DataBusSeparated NUMERIC "1"
// Retrieval info: PRIVATE: IMPLEMENT_IN_LES NUMERIC "0"
// Retrieval info: PRIVATE: INIT_FILE_LAYOUT STRING "PORT_A"
// Retrieval info: PRIVATE: INIT_TO_SIM_X NUMERIC "0"
// Retrieval info: PRIVATE: INTENDED_DEVICE_FAMILY STRING "Cyclone III"
// Retrieval info: PRIVATE: JTAG_ENABLED NUMERIC "0"
// Retrieval info: PRIVATE: JTAG_ID STRING "NONE"
// Retrieval info: PRIVATE: MAXIMUM_DEPTH NUMERIC "0"
// Retrieval info: PRIVATE: MIFfilename STRING "lab.hex"
// Retrieval info: PRIVATE: NUMWORDS_A NUMERIC "512"
// Retrieval info: PRIVATE: RAM_BLOCK_TYPE NUMERIC "0"
// Retrieval info: PRIVATE: READ_DURING_WRITE_MODE_PORT_A NUMERIC "2"
// Retrieval info: PRIVATE: RegAddr NUMERIC "1"
// Retrieval info: PRIVATE: RegData NUMERIC "1"
// Retrieval info: PRIVATE: RegOutput NUMERIC "0"
// Retrieval info: PRIVATE: SYNTH_WRAPPER_GEN_POSTFIX STRING "0"
// Retrieval info: PRIVATE: SingleClock NUMERIC "1"
// Retrieval info: PRIVATE: UseDQRAM NUMERIC "1"
// Retrieval info: PRIVATE: WRCONTROL_ACLR_A NUMERIC "0"
// Retrieval info: PRIVATE: WidthAddr NUMERIC "9"
// Retrieval info: PRIVATE: WidthData NUMERIC "32"
// Retrieval info: PRIVATE: rden NUMERIC "0"
// Retrieval info: LIBRARY: altera_mf altera_mf.altera_mf_components.all
// Retrieval info: CONSTANT: CLOCK_ENABLE_INPUT_A STRING "BYPASS"
// Retrieval info: CONSTANT: CLOCK_ENABLE_OUTPUT_A STRING "BYPASS"
// Retrieval info: CONSTANT: INIT_FILE STRING "lab.hex"
// Retrieval info: CONSTANT: INTENDED_DEVICE_FAMILY STRING "Cyclone III"
// Retrieval info: CONSTANT: LPM_HINT STRING "ENABLE_RUNTIME_MOD=NO"
// Retrieval info: CONSTANT: LPM_TYPE STRING "altsyncram"
// Retrieval info: CONSTANT: NUMWORDS_A NUMERIC "512"
// Retrieval info: CONSTANT: OPERATION_MODE STRING "SINGLE_PORT"
```

```
// Retrieval info: CONSTANT: OUTDATA_ACLR_A STRING "NONE"
// Retrieval info: CONSTANT: OUTDATA_REG_A STRING "UNREGISTERED"
// Retrieval info: CONSTANT: POWER_UP_UNINITIALIZED STRING "FALSE"
// Retrieval info: CONSTANT: READ_DURING_WRITE_MODE_PORT_A STRING "DONT_CARE"
// Retrieval info: CONSTANT: WIDTHAD_A NUMERIC "9"
// Retrieval info: CONSTANT: WIDTH_A NUMERIC "32"
// Retrieval info: CONSTANT: WIDTH_BYTEENA_A NUMERIC "1"
// Retrieval info: USED_PORT: address 0 0 9 0 INPUT NODEFVAL "address[8..0]"
// Retrieval info: USED_PORT: clock 0 0 0 0 INPUT VCC "clock"
// Retrieval info: USED_PORT: data 0 0 32 0 INPUT NODEFVAL "data[31..0]"
// Retrieval info: USED_PORT: q 0 0 32 0 OUTPUT NODEFVAL "q[31..0]"
// Retrieval info: USED_PORT: wren 0 0 0 0 INPUT NODEFVAL "wren"
// Retrieval info: CONNECT: @address_a 0 0 9 0 address 0 0 9 0
// Retrieval info: CONNECT: @clock0 0 0 0 0 clock 0 0 0 0
// Retrieval info: CONNECT: @data_a 0 0 32 0 data 0 0 32 0
// Retrieval info: CONNECT: @wren_a 0 0 0 0 wren 0 0 0 0
// Retrieval info: CONNECT: q 0 0 32 0 @q_a 0 0 32 0
// Retrieval info: GEN_FILE: TYPE_NORMAL ram1.v TRUE
// Retrieval info: GEN_FILE: TYPE_NORMAL ram1.inc FALSE
// Retrieval info: GEN_FILE: TYPE_NORMAL ram1.cmp FALSE
// Retrieval info: GEN_FILE: TYPE_NORMAL ram1.bsf FALSE
// Retrieval info: GEN_FILE: TYPE_NORMAL ram1_inst.v FALSE
// Retrieval info: GEN_FILE: TYPE_NORMAL ram1_bb.v TRUE
// Retrieval info: LIB_FILE: altera_mf
```

PC

```
module pc #(parameter VAL = 0)(
    input clock,
    input clear,
    input enable,
    input incPC,
    input branch,
    input [31:0] BusMuxOut,
    output [31:0] BusMuxIn
);

reg [31:0] q;
initial q = VAL;

// Behavioral section for writing to the register
always @ (posedge clock)
begin
    if(clear) begin
        q <= 32'b0;
    end
end
```

```

        end
        else if(enable) begin
            q <= BusMuxOut;
        end
        else if(incPC) begin
            q <= q + 1;
        end
        else if(branch) begin
            q <= q + BusMuxOut;
        end
    end
end

assign BusMuxIn = q;

endmodule

```

Bus

```

module bus(input [31:0] BusMuxInR0, input [31:0] BusMuxInR1, input [31:0] BusMuxInR2, input [31:0] BusMuxInR3, input [31:0] BusMuxInR4, input [31:0] BusMuxInR5, input [31:0] BusMuxInR6, input [31:0] BusMuxInR7, input [31:0] BusMuxInR8, input [31:0] BusMuxInR9, input [31:0] BusMuxInR10, input [31:0] BusMuxInR11, input [31:0] BusMuxInR12, input [31:0] BusMuxInR13, input [31:0] BusMuxInR14, input [31:0] BusMuxInR15, input [31:0] BusMuxInHi, input [31:0] BusMuxInLo, input [31:0] BusMuxInZHi, input [31:0] BusMuxInZLo, input [31:0] BusMuxInPC, input [31:0] BusMuxInMDR, input [31:0] BusMuxInRInP, input [31:0] BusMuxInRCSign, input R0out, input R1out, input R2out, input R3out, input R4out, input R5out, input R6out, input R7out, input R8out, input R9out, input R10out, input R11out, input R12out, input R13out, input R14out, input R15out, input HIout, input LOout, input Zhighout, input Zlowout, input PCout, input MDRout, input InPortout, input Cout, output [31:0] BusMuxOut);

reg [31:0] out;

always @ (*) begin
    // R0out or R1out or R2out or R4out or R5out or R6out or R7out or R8out or R9out or R10out or R11out or R12out or R13out or R14out or R15out or MDRout or PCout or HIout or LOout or Zhighout or Zlowout or InPortout or Cout
    if(R0out) begin
        out = BusMuxInR0;
    end
    else if(Cout) begin
        out = BusMuxInRCSign;
    end
end

```

```
else if(R1out) begin
    out = BusMuxInR1;
end
else if(R2out) begin
    out = BusMuxInR2;
end
else if(R3out) begin
    out = BusMuxInR3;
end
else if(R4out) begin
    out = BusMuxInR4;
end
else if(R5out) begin
    out = BusMuxInR5;
end
else if(R6out) begin
    out = BusMuxInR6;
end
else if(R7out) begin
    out = BusMuxInR7;
end
else if(R8out) begin
    out = BusMuxInR8;
end
else if(R9out) begin
    out = BusMuxInR9;
end
else if(R10out) begin
    out = BusMuxInR10;
end
else if(R11out) begin
    out = BusMuxInR11;
end
else if(R12out) begin
    out = BusMuxInR12;
end
else if(R13out)begin
    out = BusMuxInR13;
end
else if(R14out)begin
    out = BusMuxInR14;
end
else if(R15out)begin
    out = BusMuxInR15;
end
```



```

    else if(HIout)begin
        out = BusMuxInHi;
    end
    else if(LOout)begin
        out = BusMuxInLo;
    end
    else if(Zhighout)begin
        out = BusMuxInZHi;
    end
    else if(Zlowout)begin
        out = BusMuxInZLo;
    end
    else if(PCout)begin
        out = BusMuxInPC;
    end
    else if(MDRout)begin
        out = BusMuxInMDR;
    end
    else if(InPortout)begin
        out = BusMuxInRInP;
    end
    // else if(Cout) begin
    //     out = BusMuxInRCSign;
    // end
    else begin
        out = 32'bx;
    end
end
assign BusMuxOut = out;
endmodule

```

ALU

```

module ALU(
    input [4:0] aluControl,
    input [31:0] BusMuxInY,
    input [31:0] BusMuxOut,
    output [31:0] Zlowout,
    output [31:0] Zhighout
);

//have two outputs instead
//reg [4:0] aluControl;
reg [31:0] COut;
reg [31:0] temp;

```

```

reg [31:0] temp1;
reg [31:0] temp2;
wire [63:0] ZOut;
integer i;

boothmult Mult(ZOut, BusMuxInY, BusMuxOut);

always @ (*) begin

    // aluControl = Operator[31:27];

    temp1 = BusMuxOut;
    temp2 = BusMuxInY;
    if(aluControl == 5'b00011) begin //Add
        COut = BusMuxInY + BusMuxOut;
    end
    else if(aluControl == 5'b00100) begin //Sub
        COut = BusMuxInY - BusMuxOut;
    end
    else if(aluControl == 5'b00101) begin //Shift Right
        for (i = 0 ; i < 31 ; i = i + 1) begin
            COut[i] = BusMuxInY[i+1];
        end
        COut[31] = 0;
    end
    else if(aluControl == 5'b00110) begin //Shift Left
        for (i = 1 ; i < 32 ; i = i + 1) begin
            COut[i] = BusMuxInY[i-1];
        end
        COut[0] = 0;
    end
    else if(aluControl == 5'b00111) begin //Rotate Right
        for (i = 0 ; i < 31 ; i = i + 1) begin
            COut[i] = BusMuxInY[i+1];
        end
        COut[31] = BusMuxInY[0];
    end
    else if(aluControl == 5'b01000) begin //Rotate Left
        for (i = 1 ; i < 32 ; i = i + 1) begin
            COut[i] = BusMuxInY[i-1];
        end
        COut[0] = BusMuxInY[31];
    end
    else if(aluControl == 5'b01001) begin //AND
        //loop with for loop, then use logical and for each bit

```

```

        for (i = 0 ; i < 32 ; i = i + 1) begin
            COut = (BusMuxInY & temp1);
        end
    end
else if(aluControl == 5'b01010) begin //OR
    for (i = 0 ; i < 32 ; i = i + 1) begin
        COut[i] = BusMuxInY[i] | BusMuxOut[i];
    end
end
else if(aluControl == 5'b01110) begin //Multiply
    COut = ZOut[31:0];
    temp = ZOut[63:32];
end
else if(aluControl == 5'b01111) begin //Divide
    COut = BusMuxInY / BusMuxOut;
end
else if(aluControl == 5'b10000) begin // Negate
    for (i = 0 ; i < 32 ; i = i + 1) begin
        COut[i] = ~temp1[i];
    end
    COut[0] = COut[0] + 1'b1;
end
else if(aluControl == 5'b10001) begin // Not
    for (i = 0 ; i < 32 ; i = i + 1) begin
        COut[i] = ~temp1[i];
    end
end
    if(aluControl != 5'b01111)
        temp = {32{COut[31]}};
    // assign the results to z high and z low
end

assign Zhighout = temp; // ZOut[31:0]
assign Zlowout = COut; // ZOut[63:32]

endmodule

// Z register holds the results of the operation in ALU

```

Testbenches and Simulation runs

Note that for all testbenches, steps T0-T2 are used to fetch the instruction from memory at address 0 by preloading the value of 0 in the PC (PCout = 1 and MARIn=1 to store address 0 in MAR for memory access of ram). Read and MDRIn are set to 1 in order to store the instruction,

which is then transferred to the IR via the bus (MDRout=1 and IRin=1). The instruction bit pattern is displayed by the contents of IR in all signal printouts.

Load Instruction – ld R1, \$85

In this case, we are preloading the value of 0 into R0. The select and encode module sets R0out to 1 in order to retrieve the value and store it into the Y register to compute the addition with the sign extended value 85. The result is then sent to the MAR via the bus to perform a memory read at the address 0x55 computed (85 in decimal). To verify, we placed a value of 1 at that address and checked that R1 contained 1.

```
`timescale 1ns/10ps

module memtb;
    reg PCout, Zlowout, MDRout; // add any other signals to see in your simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b1010, T4= 4'b1011, T5=
4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, incPC, Read, Write, Operator, clk,
clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout);

    initial begin
        clk = 0;
        forever #10 clk = ~clk;
    end

    always @(posedge clk) //finite state machine; if clk rising-edge
    begin
        case (Present_state)
            Default : #40 Present_state = T0;
            T0      : #40 Present_state = T1;
            T1      : #40 Present_state = T2;
            T2      : #40 Present_state = T3;
            T3      : #40 Present_state = T4;
            T4      : #40 Present_state = T5;
            T5      : #40 Present_state = T6;
            T6      : #40 Present_state = T7;
        endcase
    end
```

```

end

always @(Present_state) // do the required job in each state
begin
    case (Present_state) //assert the required signals in each clk cycle
        Default: begin
            PCout <= 0; Zlowout <= 0; MDRout<= 0; //initialize the signals
            MARin <= 0; Zin <= 0;
            PCin <=0; MDRin <= 0; IRin <= 0; Yin <= 0;
            incPC <= 0; Read <= 0; Operator <= 5'b000000;
            Gra<= 0; Grb<= 0; Grc<= 0; Rin<= 0; Rout<= 0; BAout<= 0; Cout<=0;
            clear <= 1; //initialize registers to 0
            #10 clear <= 0;
        end

        T0: begin
            //load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1; //incPC <= 1; Zin <= 1; used to inc PC by 4
        end

        T1: begin
            //Zlowout <= 1; PCin <= 1;
            PCout <= 0;
            //MDR will grab value from ram @ address 0, this address should contain instruction
            #5 Read <= 1;
            #5 MDRin <= 1;
        end

        end

        T2: begin
            Read <= 0;
            MARin <= 0;
            MDRin <= 0;
            //load MDR value to bus which contains instruction, instruction is then stored in IR
            MDRout<= 1; IRin <= 1;
        end

        end

        T3: begin
            MDRout<= 0;
            IRin <= 0;
            //select R0out since Rb = 0000
            Grb <= 1;
            //set to 1 to generate R0out = 1 and store value of R0 (0) into Y register
            BAout <= 1;
            Yin <= 1;
            #5 Grb <= 0;
        end

        end

        T4: begin

```

```

        BAout <= 0;
        Yin <= 0;
        //store C sign extended value on bus (should be 85 decimal)
        Cout <=1;
        //perform add between 85/BuxMuxOut + R0 (0)/BuxMuxInY
        Operator <= 5'b00011;
        //store result in Z register
        Zin <=1;

    end

    //read from ram
    T5: begin
        Cout <= 0;
        Zin <=0;
        // Grb <= 0;

        //store Z register contents (85) in bus
        Zlowout <= 1;

        //load 85/busMuxOut into MAR to get address of 85
        MARin <= 1;

    end

    T6: begin
        Zlowout <=0;
        MARin<=0;
        //read from ram at address 85 and load that value in MDR -> we will need to have a preset value in memory
        //at address 85
        Read <= 1;
        MDRin <= 1;


    end

    T7: begin
        Read <= 0;
        MDRin <= 0;
        //load value in MDR on Bus
        MDRout <= 1;
        //set R1in signal to 1, value that was in memory at address 85 should now be stored in R1
        Gra <= 1; //RA in Selectencode should be 0001 in binary
        Rin <= 1;

    end

endcase
end
endmodule

```

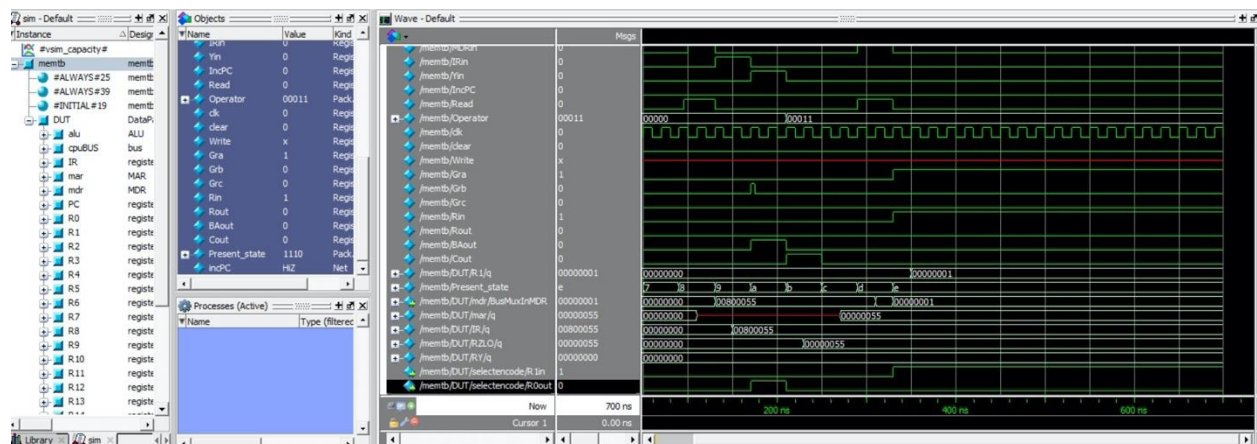

Load Instruction – ld R0, \$35(R1)

In this case, we are preloading the value of 5 into R1. The select and encode module sets R1out to 1 in order to retrieve the value and store it into the Y register to compute the addition with the sign extended value 35. The result is then sent to the MAR via the bus to perform a memory read at the address 0x28 computed (40 in decimal). To verify, we placed a value of 1 at that address and checked that R0 contained 1.

```

`timescale 1ns/10ps

module memtb;
    reg PCout, Zlowout, MDROUT, R2out, R4out;
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b1010, T4= 4'b1011, T5=
4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDROUT, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Write, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout);

    initial begin
        clk = 0;
        forever #10 clk = ~clk;
    end

    always @(posedge clk) //finite state machine; if clk rising-edge
    begin
        case (Present_state)

```

```

Default    : #40 Present_state = T0;
T0         : #40 Present_state = T1;
T1         : #40 Present_state = T2;
T2         : #40 Present_state = T3;
T3         : #40 Present_state = T4;
T4         : #40 Present_state = T5;
T5         : #40 Present_state = T6;
T6         : #40 Present_state = T7;
endcase
end

always @(Present_state) // do the required job in each state
begin
    case (Present_state) //assert the required signals in each clk cycle
        Default: begin
            PCout <= 0; Zlowout <= 0; MDRout <= 0; //initialize the signals
            MARin <= 0; Zin <= 0;
            PCin <= 0; MDRin <= 0; IRin <= 0; Yin <= 0;
            incPC <= 0; Read <= 0; Operator <= 5'b000000;
            Gra <= 0; Grb <= 0; Grc <= 0; Rin <= 0; Rout <= 0; BAout <= 0; Cout <= 0;
            clear <= 1; //initialize registers to 0
            #10 clear <= 0;
        end

        T0: begin
            //load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1;
        end

        T1: begin
            PCout <= 0;
            //MDR will grab value from ram @ address 0, this address should contain instruction
            #5 Read <= 1;
            #5 MDRin <= 1;
        end

        end

        T2: begin
            Read <= 0;
            MARin <= 0;
            MDRin <= 0;
            //load MDR value to bus which contains instruction, instruction is then stored in IR
            MDRout <= 1; IRin <= 1;
        end

        end

        T3: begin
            MDRout <= 0;
            IRin <= 0;
            //select R1out since Rb = 0001

```



```

    Grb <= 1;
    //set to 1 to generate R1out = 1 and store value of R1 (5 decimal) into Y register
    BAout <= 1;
    Yin <= 1;
    #5 Grb <= 0;
end

T4: begin
    BAout <= 0;
    Yin <= 0;
    //store C sign extended value on bus (should be 35 decimal)
    Cout <= 1;
    //perform add between 35/BuxMuxOut + R1 (5)/BuxMuxInY
    Operator <= 5'b00011;
    //store result in Z register
    Zin <= 1;

end

//read from ram
T5: begin
    Cout <= 0;
    Zin <= 0;

    //store Z register contents (40) in bus
    Zlowout <= 1;

    //load 40/busMuxOut into MAR to get address of 40
    MARin <= 1;


end

T6: begin
    Zlowout <= 0;
    MARin <= 0;
    //read from ram at address 40 and load that value in MDR -> we will need to have a preset value in memory
    //at address 40
    Read <= 1;
    MDRin <= 1;

end

T7: begin
    Read <= 0;
    MDRin <= 0;
    //load value in MDR on Bus
    MDRout <= 1;
    //set R0in signal to 1, value that was in memory at address 40 should now be stored in R1

```

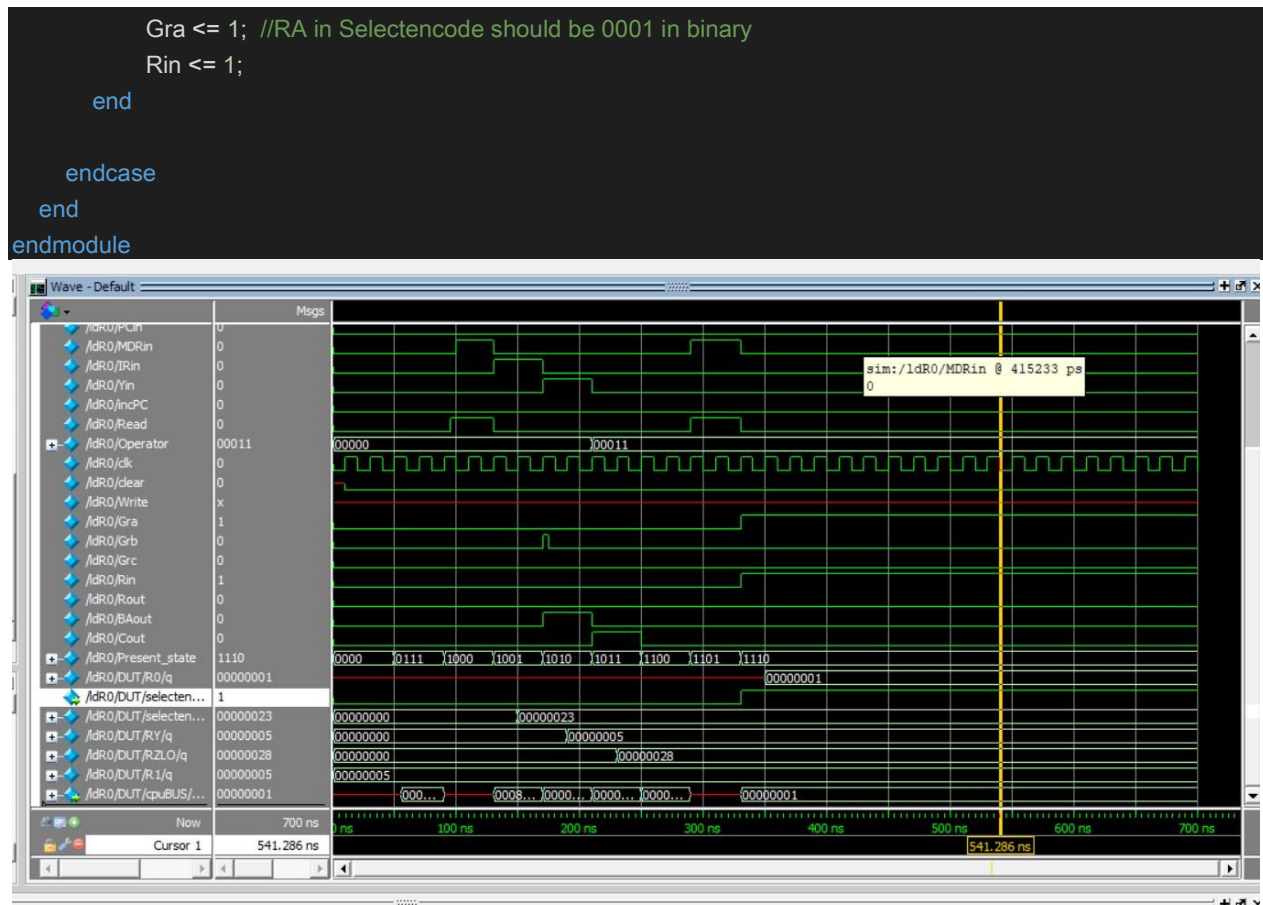

Load Instruction – ldi R1, \$85

The testbench written to test this instruction required less steps as the value in the instruction is directly loaded to register R1. That is, the C sign extended value contains 0x55 (85), Gra and Rin =1 to isolate the four bits in the instruction that correspond to 0001 to set R1in to 1 and load the immediate value 0x55 in R1. The results clearly indicate that R1 contains 0x55 (85) after the fifth cycle.

```

`timescale 1ns/10ps

module ldiR1;
    reg PCout, Zlowout, MDRout, R2out, R4out; // add any other signals to see in your simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b1010, T4= 4'b1011, T5=
    4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

```

DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Write, Operator, clk, clear, Gra, Grb, Grc, Rin, Rout, BAout,Cout);

initial begin

clk = 0;

forever #10 clk = ~clk;

end

always @(posedge clk) //finite state machine; if clk rising-edge

begin

case (Present_state)

Default : #40 Present_state = T0;

T0 : #40 Present_state = T1;

T1 : #40 Present_state = T2;

T2 : #40 Present_state = T3;

T3 : #40 Present_state = T4;

T4 : #40 Present_state = T5;

endcase

end

always @(Present_state) // do the required job ineach state

begin

case (Present_state) //assert the required signals in each clk cycle

Default: begin

PCout <= 0; Zlowout <= 0; MDRout<= 0; //initialize the signals

MARin <= 0; Zin <= 0;

PCin <=0; MDRin <= 0; IRin <= 0; Yin <= 0;

incPC <= 0; Read <= 0; Operator <= 5'b00000;

Gra<= 0; Grb<= 0; Grc<= 0; Rin<= 0; Rout<= 0; BAout<= 0; Cout<=0;

clear <= 1; //initialize registers to 0

#10 clear <= 0;

end

T0: begin

//load value in PC register (0) in MAR

#5 PCout <= 1;

#5 MARin <= 1; //IncPC <= 1; Zin <= 1; used to inc PC by 4

end

T1: begin

//Zlowout <= 1; PCin <= 1;

PCout <= 0;

//MDR will grab value from ram @ address 0, this address should contain instruction

#5 Read <= 1;

#5 MDRin <= 1;

end

```

T2: begin
    Read <= 0;
    MARin <= 0;
    MDRin <= 0;
    //load MDR value to bus which contains instruction, instruction is then stored in IR
    MDRout<= 1; IRin <= 1;
end

T3: begin
    MDRout<= 0;
    IRin <= 0;
    //select R0out since Rb = 0000
    Grb <= 1;
    //set to 1 to generate R0out = 1
    BAout <= 1;
    Yin <= 1;
    #5 Grb <= 0;
end

T4: begin
    BAout <= 0;
    Yin <= 0;
    //store C sign extended value on bus (should be 85 decimal)
    Cout <=1;
    //perform add between 85/BuxMuxOut + R0 (0)/BuxMuxInY
    Operator <= 5'b00011;
    //store result in Z register
    Zin <=1;

end


//read from ram
T5: begin
    Cout <= 0;
    Zin <=0;

    //store Z register contents (85) in bus
    Zlowout <= 1;
    Gra <= 1; //RA in Selectencode should be 0001 in binary
    Rin <= 1;

end

endcase
end
endmodule

```

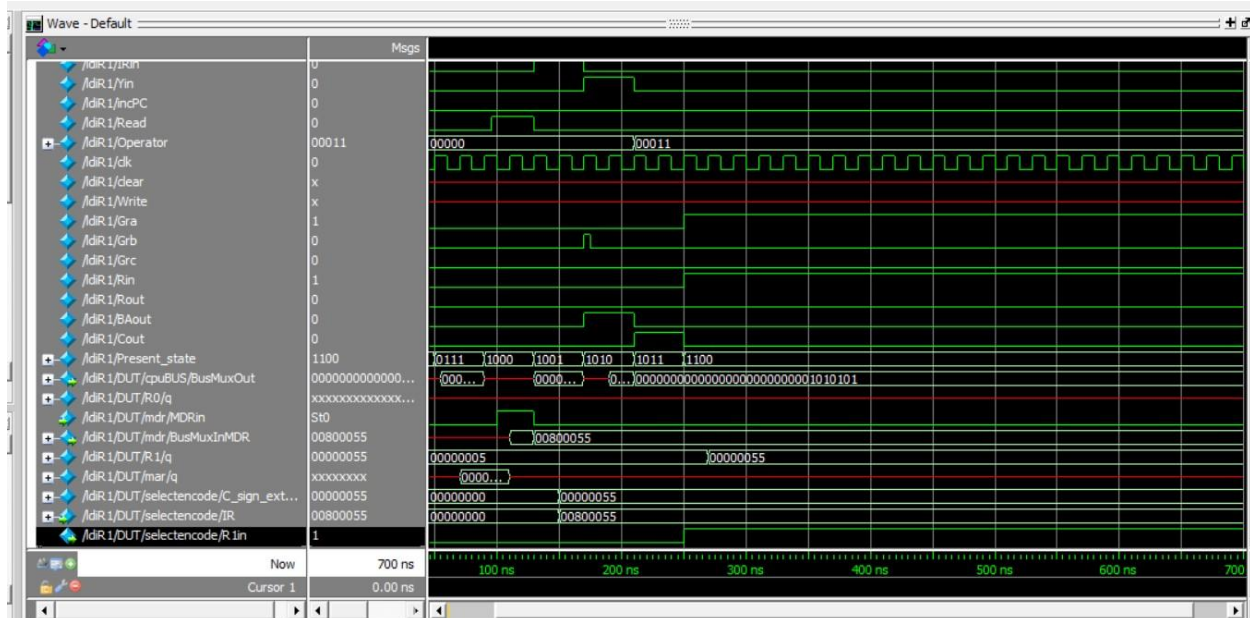

Load Instruction – ldi R0, \$35(R1)

This load instruction loads the immediate value that is the sum of the contents of R1 and 35. That is, the C sign extended value contains 0x23 (35) and R1 was preloaded with the value 5. To validate this test, we verified that R0 contained 0x28.

```
*timescale 1ns/10ps

module ldiR0;
    reg PCout, Zlowout, MDRout, R2out, R4out; // add any other signals to see in your simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b1010, T4= 4'b1011, T5=
4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Write, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout);

    initial begin
        clk = 0;
        forever #10 clk = ~clk;
    end
end
```

```

always @(posedge clk)    //finite state machine; if clk rising-edge
begin
    case (Present_state)
        Default    : #40 Present_state = T0;
        T0         : #40 Present_state = T1;
        T1         : #40 Present_state = T2;
        T2         : #40 Present_state = T3;
        T3         : #40 Present_state = T4;
        T4         : #40 Present_state = T5;
    endcase
end

always @(Present_state)  // do the required job in each state
begin
    case (Present_state)    //assert the required signals in each clk cycle
        Default: begin
            PCout <= 0; Zlowout <= 0; MDRout <= 0; //initialize the signals
            MARin <= 0; Zin <= 0;
            PCin <= 0; MDRin <= 0; IRin <= 0; Yin <= 0;
            incPC <= 0; Read <= 0; Operator <= 5'b000000;
            Gra <= 0; Grb <= 0; Grc <= 0; Rin <= 0; Rout <= 0; BAout <= 0; Cout <= 0;
            clear <= 1; //initialize registers to 0
            #10 clear <= 0;
        end

        T0: begin
            //load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1; //IncPC <= 1; Zin <= 1; used to inc PC by 4
        end

        T1: begin
            //Zlowout <= 1; PCin <= 1;
            PCout <= 0;
            //MDR will grab value from ram @ address 0, this address should contain instruction
            #5 Read <= 1;
            #5 MDRin <= 1;

        end

        T2: begin
            Read <= 0;
            MARin <= 0;
            MDRin <= 0;
            //load MDR value to bus which contains instruction, instruction is then stored in IR
            MDRout <= 1; IRin <= 1;
        end
    endcase
end

```

```

T3: begin
    MDRout<= 0;
    IRin <= 0;
    Grb <= 1;
    //set to 1 to generate R1out = 1 and store value of R1 (5 hex) into Y register
    BAout <= 1;
    Yin <= 1;
    #5 Grb <= 0;
end

T4: begin
    BAout <= 0;
    Yin <= 0;
    //store C sign extended value on bus (should be 35 decimal)
    Cout <=1;
    //perform add between 35/BuxMuxOut + R1 (5)/BuxMuxInY
    Operator <= 5'b00011;
    //store result in Z register
    Zin <=1;

end

//read from ram
T5: begin
    Cout <= 0;
    Zin <=0;


    //store Z register contents (85) in bus
    Zlowout <= 1;
    Gra <= 1; //RA in Selectencode should be 0000 in binary
    Rin <= 1;

end

//roin, r1out, y register, csignextended, z register, r1, r0

endcase
end
endmodule

```

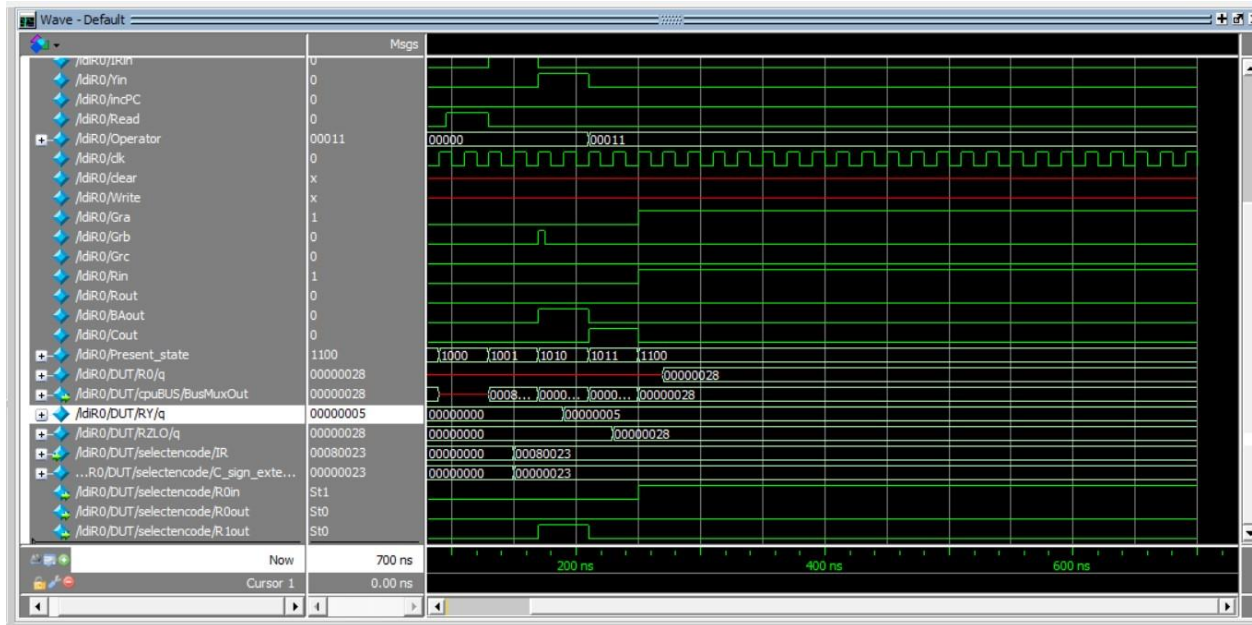

Store Instruction – st \$90, R1

This instruction verifies that the design can write the contents of R1 to the address 90 in ram. After loading the instruction into IR (T0-T2), the address is computed (90 + contents of R0 which are 0). Once the address is stored into the MAR and the value of R1 is transferred to MDR via the bus, the write signal is set to 1 to perform a memory write. Since R1 was preloaded with 5, we verified the memory contents at address 0x5A.

```
`timescale 1ns/10ps

module store;
    reg PCout, Zlowout, MDRout, R2out, R4out; // add any other signals to see in your simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b1010, T4= 4'b1011, T5=
4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Write, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout);

    initial begin
        clk = 0;
        forever #10 clk = ~clk;
    end
end
```



```

always @(posedge clk)    //finite state machine; if clk rising-edge
begin
    case (Present_state)
        Default    : #40 Present_state = T0;
        T0         : #40 Present_state = T1;
        T1         : #40 Present_state = T2;
        T2         : #40 Present_state = T3;
        T3         : #40 Present_state = T4;
        T4         : #40 Present_state = T5;
        T5         : #40 Present_state = T6;
        T6         : #40 Present_state = T7;
    endcase
end

always @(Present_state)  // do the required job in each state
begin
    case (Present_state)    //assert the required signals in each clk cycle
        Default: begin
            PCout <= 0; Zlowout <= 0; MDRout <= 0; //initialize the signals
            MARin <= 0; Zin <= 0;
            PCin <= 0; MDRin <= 0; IRin <= 0; Yin <= 0;
            incPC <= 0; Read <= 0; Operator <= 5'b000000;
            Gra <= 0; Grb <= 0; Grc <= 0; Rin <= 0; Rout <= 0; BAout <= 0; Cout <= 0;
            clear <= 0;
        end

        T0: begin
            //load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1; //IncPC <= 1; Zin <= 1; used to inc PC by 4
        end

        T1: begin
            //Zlowout <= 1; PCin <= 1;
            PCout <= 0;
            //MDR will grab value from ram @ address 0, this address should contain instruction
            #5 Read <= 1;
            #5 MDRin <= 1;
        end

        T2: begin
            Read <= 0;
            MARin <= 0;
            MDRin <= 0;
            //load MDR value to bus which contains instruction, instruction is then stored in IR
            MDRout <= 1; IRin <= 1;
        end

        T3: begin

```

```

MDRout<= 0;
IRin <= 0;
//select R0out since Rb = 0000
Grb <= 1;
//set to 1 to generate R0out = 1 and store value of R0 (0 hex) into Y register
BAout <= 1;
Yin <= 1;
#5 Grb <= 0;
end

```

```

T4: begin
  BAout <= 0;
  Yin <= 0;
  //store C sign extended value on bus (should be 90 decimal)
  Cout <=1;
  //perform add between 90/BuxMuxOut + R0 (0)/BuxMuxInY
  Operator <= 5'b00011;
  //store result in Z register
  Zin <=1;

end

```

```

T5: begin
  Cout <= 0;
  Zin <=0;

  //store Z register contents (85) in bus
  Zlowout <= 1;

  //load 90/busMuxOut into MAR to get address of 85
  MARin <= 1;

end

```

```

T6: begin
  Zlowout <=0;
  MARin<=0;
  Gra <= 1; //RA in Selectencode should be 0001 in binary
  BAout <= 1;
  MDRin <= 1; //load value of 85 from R1 to MDR

end

```

```

T7: begin
  MDRin <= 0;
  Gra <= 0;
  BAOout <=0;
  Write <= 1;



```

```

end

endcase
end
endmodule

```

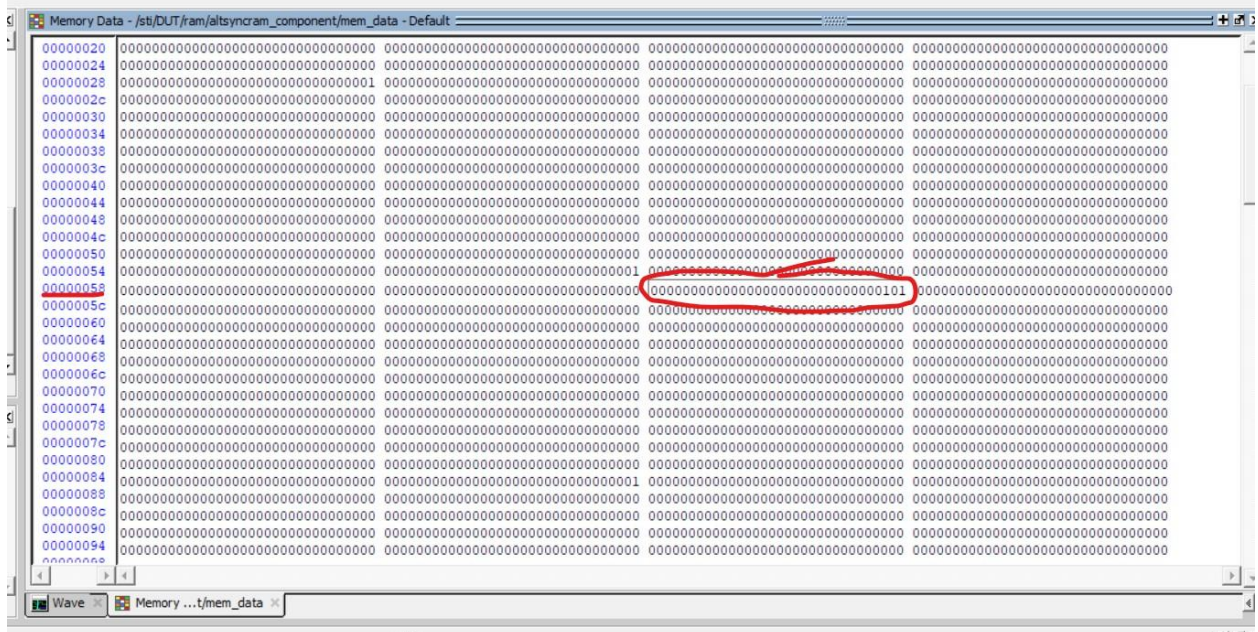 

Store Instruction – st \$90(R1), R1

This instruction follows the same steps as the previous test except that the address is calculated by adding 90 with the value stored in R1 (5). Therefore, we verified that 5 was written at address 0x5f.

```

`timescale 1ns/10ps

module storeidx;
    reg PCout, Zlowout, MDRout, R2out, R4out; // add any other signals to see in your simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b1010, T4= 4'b1011, T5=
4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Write, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout);

    initial begin
        clk = 0;
        forever #10 clk = ~clk;
    end

    always @(posedge clk) //finite state machine; if clk rising-edge
    begin
        case (Present_state)
            Default : #40 Present_state = T0;
            T0      : #40 Present_state = T1;
            T1      : #40 Present_state = T2;
            T2      : #40 Present_state = T3;
            T3      : #40 Present_state = T4;
            T4      : #40 Present_state = T5;
            T5      : #40 Present_state = T6;
            T6      : #40 Present_state = T7;
        endcase
    end

    always @(Present_state) // do the required job in each state
    begin
        case (Present_state) //assert the required signals in each clk cycle
            Default: begin
                PCout <= 0; Zlowout <= 0; MDRout <= 0; //initialize the signals
                MARin <= 0; Zin <= 0;
                PCin <= 0; MDRin <= 0; IRin <= 0; Yin <= 0;
                incPC <= 0; Read <= 0; Operator <= 5'b00000;
                Gra <= 0; Grb <= 0; Grc <= 0; Rin <= 0; Rout <= 0; BAout <= 0; Cout <= 0;
            end
        endcase
    end
end

```

```

    clear <= 0;
end

T0: begin
    //load value in PC register (0) in MAR
    #5 PCout <= 1;
    #5 MARin <= 1; //IncPC <= 1; Zin <= 1; used to inc PC by 4
end

T1: begin
    //Zlowout <= 1; PCin <= 1;
    PCout <= 0;
    //MDR will grab value from ram @ address 0, this address should contain instruction
    #5 Read <= 1;
    #5 MDRin <= 1;

end

T2: begin
    Read <= 0;
    MARin <= 0;
    MDRin <= 0;
    //load MDR value to bus which contains instruction, instruction is then stored in IR
    MDRout<= 1; IRin <= 1;
end

T3: begin
    MDRout<= 0;
    IRin <= 0;
    //select R1out since Rb = 0001
    Grb <= 1;
    //set to 1 to generate R1out = 1 and store value of R1 (85 hex) into Y register
    BAout <= 1;
    Yin <= 1;
    #5 Grb <= 0;
end

T4: begin
    BAout <= 0;
    Yin <= 0;
    //store C sign extended value on bus (should be 90 decimal)
    Cout <= 1;
    //perform add between 90/BuxMuxOut + R1 (85)/BuxMuxInY
    Operator <= 5'b00011;
    //store result in Z register
    Zin <= 1;

end

T5: begin

```

```

    Cout <= 0;
    Zin <=0;

    //store Z register contents (85) in bus
    Zlowout <= 1;

    //load 90/busMuxOut into MAR to get address of 85
    MARin <= 1;

end

T6: begin
    Zlowout <=0;
    MARin<=0;
    Grb <= 1; //RA in Selectencode should be 0001 in binary
    BAout <= 1;
    MDRin <= 1; //load value of 85 from R1 to MDR

end

T7: begin
    MDRin <= 0;
    Grb <= 0;
    BAOout <=0;
    Write <= 1;

end

endcase
end
endmodule

```


Verify Jump Case

Here we are verifying the functionality of the jr instruction by simulating the control sequence for jr R1. Note that R1 was preloaded with the value 5.

```
`timescale 1ns/10ps

module TBjumpcase;
    reg PCout, Zlowout, MDRout, R2out, R4out; // add any other signals to see in y
our simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b10
10, T4= 4'b1011, T5= 4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Wr
ite, Operator, clk, clear,
    Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn);

    initial begin
        clk = 0;
        forever #10 clk = ~clk;
    end

    always @(posedge clk) //finite state machine; if clk rising-edge
    begin
        case (Present_state)
            Default      :    #40 Present_state = T0;
            T0           :    #40 Present_state = T1;
            T1           :    #40 Present_state = T2;
            T2           :    #40 Present_state = T3;
            T3           :    #40 Present_state = T4;
            T4           :    #40 Present_state = T5;
            T5           :    #40 Present_state = T6;
            T6           :    #40 Present_state = T7;
        endcase
    end
end
```



```

always @(Present_state)    // do the required job in each state
begin
    case (Present_state)    // assert the required signals in each clock cycle
        Default: begin
            PCout <= 0;    Zlowout <= 0;    MDRout <= 0;    // initialize the signals
            MARin <= 0;    Zin <= 0;
            PCin <= 0;    MDRin <= 0;    IRin <= 0;    Yin <= 0;
            incPC <= 0;    Read <= 0;    Operator <= 5'b00000;
            Gra <= 0;    Grb <= 0;    Grc <= 0;    Rin <= 0;    Rout <= 0;    BAout <= 0;    Cout <= 0;

            // clear <= 1; // initialize registers to 0
            clear <= 0;
        end

        T0: begin
            // load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1;    // IncPC <= 1; Zin <= 1; used to inc PC by 4
        end

        T1: begin
            // Zlowout <= 1; PCin <= 1;
            PCout <= 0;
            MARin <= 0;
            // MDR will grab value from ram @ address 0, this address should contain instruction
            #5 Read <= 1;
            #5 MDRin <= 1;
        end

        T2: begin
            Read <= 0;
            MARin <= 0;
            MDRin <= 0;
            // load MDR value to bus which contains instruction, instruction is then stored in IR
            MDRout <= 1;    IRin <= 1;
        end

        T3: begin
            MDRout <= 0;
            IRin <= 0;

            Gra <= 1;

```

```

        Rout <= 1;
        PCin <= 1;
        BAout <= 1;


    end

    endcase

end

endmodule

```

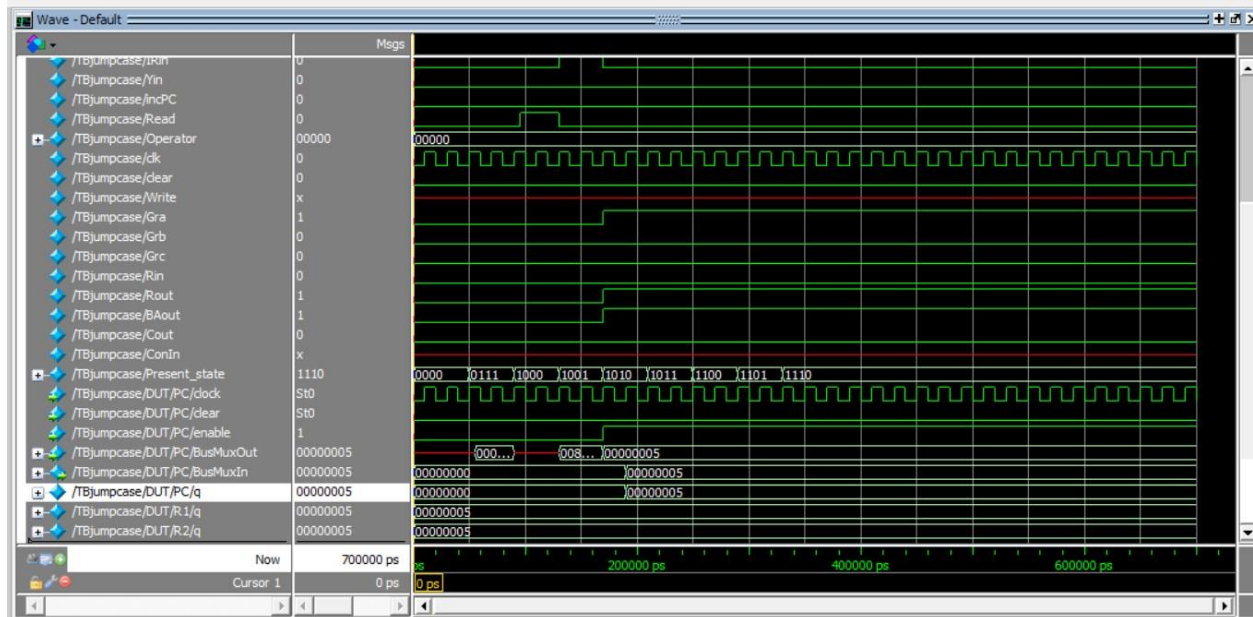

Mfhi & mflo

Here we are verifying the functionality by simulating the control sequences for mfhi R1 and mflo R1. Note that R1 was preloaded with the value 5.

```

`timescale 1ns/10ps

module TBmfhiandlo;
    reg PCout, Zlowout, MDRout, R2out, R4out; // add any other signals to see in y
our simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn, HIout;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b10
10, T4= 4'b1011, T5= 4'b1100, T6= 4'b1101, T7= 4'b1110;

```

```

    reg[3:0] Present_state= Default;

DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Write, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn, HIout);

initial begin
    clk = 0;
    forever #10 clk = ~clk;
end

always @(posedge clk)    //finite state machine; if clk rising-edge
    begin
        case (Present_state)
            Default      :   #40 Present_state = T0;
            T0           :   #40 Present_state = T1;
            T1           :   #40 Present_state = T2;
            T2           :   #40 Present_state = T3;
            T3           :   #40 Present_state = T4;
            T4           :   #40 Present_state = T5;
            T5           :   #40 Present_state = T6;
            T6           :   #40 Present_state = T7;
        endcase
    end

always @(Present_state)    // do the required job in each state
    begin
        case (Present_state)    //assert the required signals in each clock cycle
            Default: begin
                PCout <= 0;   Zlowout <= 0;   MDRout<= 0;   //initialize the signals
                MARin <= 0;   Zin <= 0;
                PCin <=0;   MDRin <= 0;   IRin  <= 0;   Yin <= 0;
                //IncPC <= 0;
                Read <= 0;   Operator <= 5'b00000;
                Gra<= 0; Grb<= 0; Grc<= 0; Rin<= 0; Rout<= 0; BAout<= 0; Cout<=0;
                #10 clear <= 0; HIout <= 0;
            end

            T0: begin
                //load value in PC register (0) in MAR
                #5 PCout <= 1;

```

```


        #5 MARin <= 1; //IncPC <= 1; Zin <= 1; used to inc PC by 4
    end
    T1: begin
        //Zlowout <= 1; PCin <= 1;
        PCout <= 0;
        MARin <= 0;
        //MDR will grab value from ram @ address 0, this address should contain instruction
        #5 Read <= 1;
        #5 MDRin <= 1;

    end
    T2: begin
        Read <= 0;
        MARin <= 0;
        MDRin <= 0;
        //load MDR value to bus which contains instruction, instruction is then stored in IR
        MDRout<= 1; IRin <= 1;
    end

    T3: begin
        MDRout <= 0;
        IRin <= 0;
        Read <= 0;
        MDRin <= 0;
        //load value in MDR on Bus
        HIout <= 1;
        //set R1in signal to 1, value that was in memory at address 85 should now be stored in R1
        Gra <= 1; //RA in Selectencode should be 0001 in binary
        Rin <= 1;

    end
endcase
end
endmodule

```

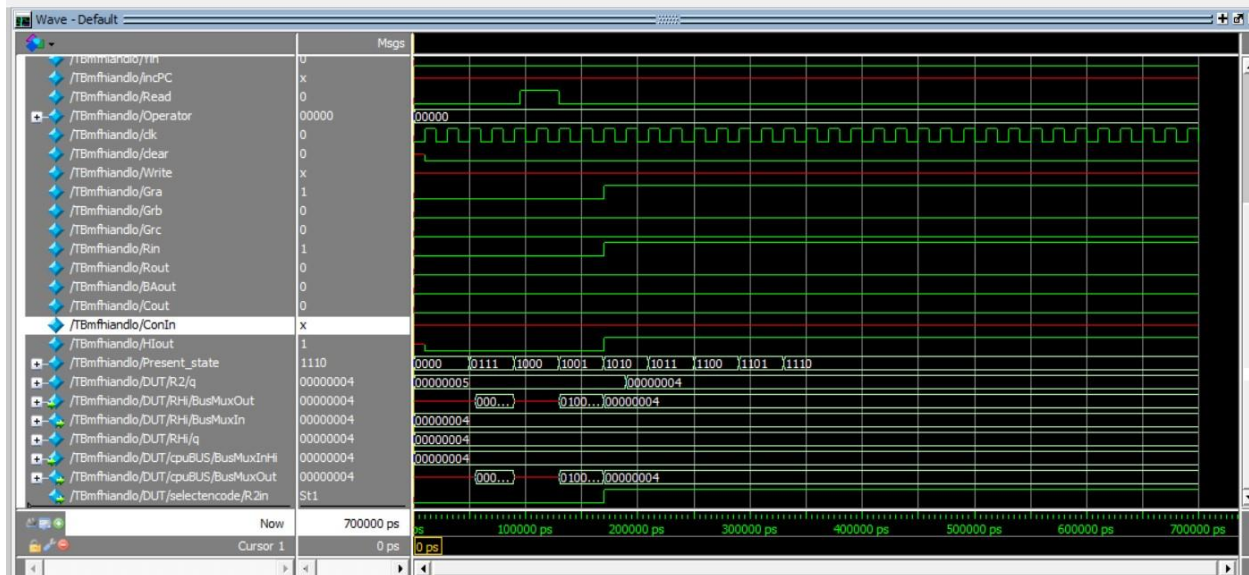

In/Out

Here we are verifying the functionality of our Output Port logic by simulating the control sequence for out R1. Note that R1 was preloaded with the value 5.

```
`timescale 1ns/10ps

module TBinout;
    reg POut, Zlowout, MDROUT, R2out, R4out; // add any other signals to see in y
our simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn, RoutPin;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3= 4'b10
10, T4= 4'b1011, T5= 4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDROUT, MARin, Zin, PCin, MDRin, IRin, Yin, Read, Wr
ite, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn, RoutPin);

    initial begin
        clk = 0;
        forever #10 clk = ~clk;
    end
```

```

always @(posedge clk)    //finite state machine; if clk rising-edge
begin
    case (Present_state)
        Default      :   #40 Present_state = T0;
        T0           :   #40 Present_state = T1;
        T1           :   #40 Present_state = T2;
        T2           :   #40 Present_state = T3;
        T3           :   #40 Present_state = T4;
        T4           :   #40 Present_state = T5;
        T5           :   #40 Present_state = T6;
        T6           :   #40 Present_state = T7;
    endcase
end

always @(Present_state)    // do the required job in each state
begin
    case (Present_state)    //assert the required signals in each c
lk cycle
        Default: begin
            PCout <= 0;   Zlowout <= 0;   MDRout<= 0;   //initialize the sign
als
            MARin <= 0;   Zin <= 0;
            PCin <=0;   MDRin <= 0;   IRin  <= 0;   Yin <= 0;
            incPC <= 0;   Read <= 0;   Operator <= 5'b00000;
            Gra<= 0; Grb<= 0; Grc<= 0; Rin<= 0; Rout<= 0; BAout<= 0; Cout<=0;
            // clear <= 1; //initialize registers to 0
            // #10 clear <= 0;
        end

        T0: begin
            //load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1;   //IncPC <= 1; Zin <= 1; used to inc PC by 4
        end

        T1: begin
            //Zlowout <= 1; PCin <= 1;
            PCout <= 0;
            //MDR will grab value from ram @ address 0, this address should co
ntain instruction
            #5 Read <= 1;
            #5 MDRin <= 1;
        end
    end
end

```


```

T2: begin
    Read <= 0;
    MARin <= 0;
    MDRin <= 0;
    //load MDR value to bus which contains instruction, instruction i
s then stored in IR
    MDRout<= 1; IRin <= 1;
end

T3: begin
    MDRout <= 0;
    IRin <= 0;

    Gra <= 1;
    Rout <= 1;
    RoutPin <= 1;
end
endcase
end
endmodule

```

 

Addi instruction – R2, R1, -5

This instruction verifies that the design can subtract 5 from the contents of R1 and store the result in R2. First the instruction into IR (T0-T2), then the add operation is performed. The result is stored in RZLo and then moved into the destination register, R2.

```
// Op-code: 31-27, Ra: 26-23, C2: 22-19, C: 18-0
```

```
`timescale 1ns/10ps
```

```
module addi_tb;  
    reg PCout, Zlowout, MDRout; // add any other signals to see in your  
simulation
```

```
    reg MARin, Zin, PCin, MDRin, IRin, Yin;  
    reg incPC, Read;  
    reg [4:0] Operator;  
    reg clk;  
    reg clear, Write;  
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn;
```

```
    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3=  
4'b1010, T4= 4'b1011, T5= 4'b1100, T6= 4'b1101, T7= 4'b1110;  
    reg[3:0] Present_state= Default;
```

```
DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read,  
Write, Operator, clk, clear,  
Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn);
```

```
initial begin  
    clk = 0;  
    forever #10 clk = ~clk;  
end
```

```
always @(posedge clk) //finite state machine; if clk rising-edge  
begin  
    case (Present_state)  
        Default      :    #40 Present_state = T0;  
        T0           :    #40 Present_state = T1;  
        T1           :    #40 Present_state = T2;  
        T2           :    #40 Present_state = T3;  
        T3           :    #40 Present_state = T4;  
        T4           :    #40 Present_state = T5;  
        T5           :    #40 Present_state = T6;  
        T6           :    #40 Present_state = T7;  
    endcase
```



```

end

always @(Present_state) // do the required job in each state
begin
    case (Present_state) // assert the required signals in each
    clk cycle
        Default: begin
            PCout <= 0; Zlowout <= 0; MDRout <= 0; // initialize the
            signals
            MARin <= 0; Zin <= 0;
            PCin <= 0; MDRin <= 0; IRin <= 0; Yin <= 0;
            incPC <= 0; Read <= 0; Operator <= 5'b00000;
            Gra <= 0; Grb <= 0; Grc <= 0; Rin <= 0; Rout <= 0; BAout <= 0;
            Cout <= 0;
            // clear <= 1; // initialize registers to 0
            // #10 clear <= 0;
        end
        T0: begin
            // load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1; // IncPC <= 1; Zin <= 1; used to inc PC by 4
            // incPC <= 1;
            // Zin <= 1;
        end
        T1: begin
            // Zlowout <= 1; PCin <= 1;
            PCout <= 0;
            // MDR will grab value from ram @ address 0, this address should
            contain instruction
            #5 Read <= 1; // Mdatain <= 1;
            #5 MDRin <= 1;
        end
        T2: begin
            Read <= 0;
            MARin <= 0;
            MDRin <= 0;
            // load MDR value to bus which contains instruction, instruction
            is then stored in IR
            MDRout <= 1; IRin <= 1;
        end
        T3: begin
            MDRout <= 0;
            IRin <= 0;
            // select R0out since Rb = 0000

```

register

```
Grb <= 1;  
//set to 1 to generate R0out = 1 and store value of R0 (0) into Y
```

```
Rout <= 1;  
Yin <= 1;  
#5 Grb <= 0;
```

end

T4: begin

```
Rout <= 0;  
Yin <= 0;  
//store C sign extended value on bus (should be 85 decimal)  
Cout <= 1;  
//perform add between 85/BuxMuxOut + R0 (0)/BuxMuxInY  
Operator <= 5'b00011; // Add  
//store result in Z register  
Zin <=1;
```

end

//read from ram

T5: begin

```
Cout <= 0;  
Zin <=0;  
// Grb <= 0;
```


```
//store Z register contents (85) in bus  
Zlowout <= 1;  
Gra <= 1;  
//load 85/busMuxOut into MAR to get address of 85  
Rin <= 1;
```

end

endcase

end

endmodule

 

Andi instruction – andi R2, R1, \$26

This instruction shows that the design can perform an and immediate operation on \$26 and the value of R1, then subsequently store the result in R2. The steps T0-T2 are executed first, performing the fetch instruction. The andi immediate instruction is performed and stored in the RZLo and moved to the appropriate destination register, R2.

```
`timescale 1ns/10ps
```

```
module andi_tb;
    reg PCout, Zlowout, MDRout; // add any other signals to see in your
simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg incPC, Read;
    reg [4:0] Operator;
    reg clk;
    reg clear, Write;
    reg Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn;

    parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3=
4'b1010, T4= 4'b1011, T5= 4'b1100, T6= 4'b1101, T7= 4'b1110;
    reg[3:0] Present_state= Default;

    DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read,
Write, Operator, clk, clear,
```

```
Gra, Grb, Grc, Rin, Rout, BAout,Cout, ConIn);
```

```
initial begin
    clk = 0;
    forever #10 clk = ~clk;
end
```

```
always @(posedge clk)    //finite state machine; if clk rising-edge
begin
    case (Present_state)
        Default      :    #40 Present_state = T0;
        T0            :    #40 Present_state = T1;
        T1            :    #40 Present_state = T2;
        T2            :    #40 Present_state = T3;
        T3            :    #40 Present_state = T4;
        T4            :    #40 Present_state = T5;
        T5            :    #40 Present_state = T6;
        T6            :    #40 Present_state = T7;
    endcase
end
```

```
always @(Present_state)    // do the required job ineach state
begin
    case (Present_state)    //assert the required signals in each
clk cycle
        Default: begin
            PCout <= 0;  Zlowout <= 0;  MDRout<= 0;  //initialize the
signals
            MARin <= 0;  Zin <= 0;
            PCin <=0;  MDRin <= 0;  IRin  <= 0;  Yin <= 0;
            incPC <= 0;  Read <= 0;  Operator <= 5'b00000;
            Gra <= 0; Grb <= 0; Grc <= 0; Rin <= 0; Rout <= 0; BAout <= 0;
            Cout <=0;

            // clear <= 1; //initialize registers to 0
            // #10 clear <= 0;
        end
        T0: begin
            //load value in PC register (0) in MAR
            #5 PCout <= 1;
            #5 MARin <= 1;  //IncPC <= 1; Zin <= 1; used to inc PC by 4
            // incPC <= 1;
            // Zin <= 1;
        end
    endcase
end
```

```

end
T1: begin
    // Zlowout <= 1; PCin <= 1;
    PCout <= 0;
    //MDR will grab value from ram @ address 0, this address should
contain instruction
    #5 Read <= 1; // Mdatain <= 1;
    #5 MDRin <= 1;

end
T2: begin
    Read <= 0;
    MARin <= 0;
    MDRin <= 0;
    //load MDR value to bus which contains instruction, instruction
is then stored in IR
    MDRout<= 1; IRin <= 1;

end
T3: begin
    MDRout<= 0;
    IRin <= 0;
    //select R0out since Rb = 0000
    Grb <= 1;
    //set to 1 to generate R0out = 1 and store value of R0 (0) into Y
register
    Rout <= 1;
    Yin <= 1;
    #5 Grb <= 0;

end

T4: begin
    Rout <= 0;
    Yin <= 0;
    //store C sign extended value on bus (should be 85 decimal)
    Cout <= 1;
    //perform add between 85/BuxMuxOut + R0 (0)/BuxMuxInY
    Operator <= 5'b00011; // Add
    //store result in Z register
    Zin <=1;

end

//read from ram

```


```

T5: begin
    Cout <= 0;
    Zin <= 0;
    // Grb <= 0;

    //store Z register contents (85) in bus
    Zlowout <= 1;
    Gra <= 1;
    //load 85/busMuxOut into MAR to get address of 85
    Rin <= 1;

end
endcase
end
endmodule

```

 

Ori instruction – ori R2, R1, \$26

This instruction shows that the design can perform an or immediate operation on \$26 and the value of R1, then subsequently store the result in R2. The steps T0-T2 are executed first, performing the fetch instruction. The or immediate instruction is performed and stored in the RZLO and moved to the appropriate destination register, R2.

```

`timescale 1ns/10ps

```

```

module ori_tb;

```

```

reg PCout, Zlowout, MDRout; // add any other signals to see in your
simulation
reg MARin, Zin, PCin, MDRin, IRin, Yin;
reg incPC, Read;
reg [4:0] Operator;
reg clk;
reg clear, Write;
reg Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn;

parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3=
4'b1010, T4= 4'b1011, T5= 4'b1100, T6= 4'b1101, T7= 4'b1110;
reg[3:0] Present_state= Default;

DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read,
Write, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn);

initial begin
    clk = 0;
    forever #10 clk = ~clk;
end

always @(posedge clk) //finite state machine; if clk rising-edge
begin
    case (Present_state)
        Default      :    #40 Present_state = T0;
        T0           :    #40 Present_state = T1;
        T1           :    #40 Present_state = T2;
        T2           :    #40 Present_state = T3;
        T3           :    #40 Present_state = T4;
        T4           :    #40 Present_state = T5;
        T5           :    #40 Present_state = T6;
        T6           :    #40 Present_state = T7;
    endcase
end

always @(Present_state) // do the required job in each state
begin
    case (Present_state) //assert the required signals in each
clk cycle

```

```

Default: begin
    PCout <= 0;  Zlowout <= 0;  MDRout<= 0;  //initialize the
signals
    MARin <= 0;  Zin <= 0;
    PCin <= 0;  MDRin <= 0;  IRin <= 0;  Yin <= 0;
    incPC <= 0;  Read <= 0;  Operator <= 5'b00000;
    Gra <= 0; Grb <= 0; Grc <= 0; Rin <= 0; Rout <= 0; BAout <= 0;
Cout <= 0;
    // clear <= 1; //initialize registers to 0
    // #10 clear <= 0;
end
T0: begin
    //load value in PC register (0) in MAR
    #5 PCout <= 1;
    #5 MARin <= 1;  //IncPC <= 1; Zin <= 1; used to inc PC by 4
    // incPC <= 1;
    // Zin <= 1;
end
T1: begin
    // Zlowout <= 1; PCin <= 1;
    PCout <= 0;
    //MDR will grab value from ram @ address 0, this address should
contain instruction
    #5 Read <= 1; // Mdatain <= 1;
    #5 MDRin <= 1;
end
T2: begin
    Read <= 0;
    MARin <= 0;
    MDRin <= 0;
    //load MDR value to bus which contains instruction, instruction
is then stored in IR
    MDRout<= 1; IRin <= 1;
end
T3: begin
    MDRout<= 0;
    IRin <= 0;
    //select R0out since Rb = 0000
    Grb <= 1;
    //set to 1 to generate R0out = 1 and store value of R0 (0) into Y
register
    Rout <= 1;
    Yin <= 1;
    #5 Grb <= 0;

```



```
end
```

```
T4: begin
```

```
    Rout <= 0;
```

```
    Yin <= 0;
```

```
    //store C sign extended value on bus (should be 85 decimal)
```

```
    Cout <= 1;
```

```
    //perform add between 85/BuxMuxOut + R0 (0)/BuxMuxInY
```

```
    Operator <= 5'b00011; // Add
```

```
    //store result in Z register
```

```
    Zin <=1;
```

```
end
```

```
//read from ram
```

```
T5: begin
```

```
    Cout <= 0;
```

```
    Zin <=0;
```

```
    // Grb <= 0;
```

```
    //store Z register contents (85) in bus
```

```
    Zlowout <= 1;
```

```
    Gra <= 1;
```

```
    //load 85/busMuxOut into MAR to get address of 85
```


```
    Rin <= 1;
```

```
end
```

```
endcase
```

```
end
```

```
endmodule
```

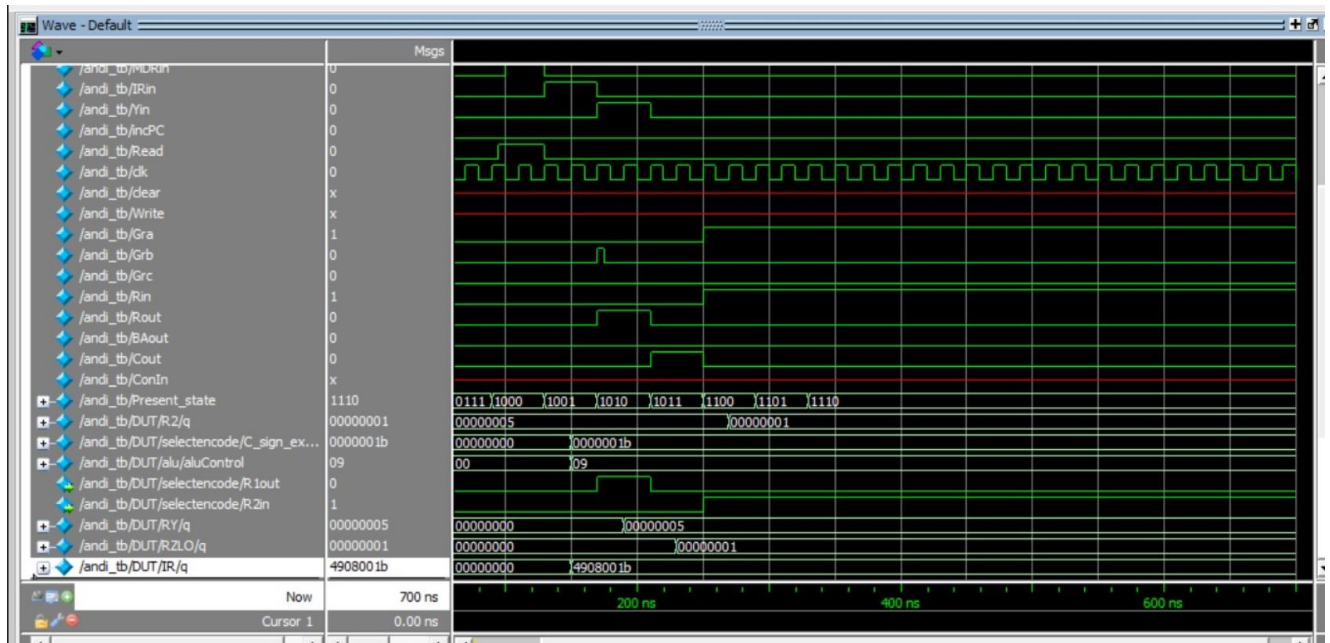

Brzr instruction – brzr R2, 35

This instruction shows that the design can perform a brzr branch (branch if zero) operation on 35 and the value of R2. The steps T0-T2 are executed first, performing the fetch instruction. Then, an operation is performed to determine whether or not to branch. If required, the branch is then performed.

```
// make tbs for:
// branch instructions: brzr, brnz, brpl, brmi
// Op-code: 31-27, Ra: 26-23, C2: 22-19, C: 18-0
// brzr: 0108 0023, C2: 0001
// 0 0000, 0010, 0001, 000 0000 0000 0010 0011
// brnz: 0110 0023, C2: 0010
// 0 0000, 0010, 0010, 000 0000 0000 0010 0011
// brpl: 0120 0023, C2: 0100
// brmi: 0140 0023, C2: 1000
```

```
`timescale 1ns/10ps
```

```
module branch_tb;
    reg PCout, Zlowout, MDRout, R2out, R4out; // add any other signals to see in your simulation
    reg MARin, Zin, PCin, MDRin, IRin, Yin;
    reg Read;
    reg [4:0] Operator;
    reg clk;
```

```

reg clear, Write;
reg Gra, Grb, Grc, Rin, Rout, BAout, Cout;
reg ConIn;

parameter Default = 4'b0000, T0= 4'b0111, T1= 4'b1000, T2= 4'b1001, T3=
4'b1010, T4= 4'b1011, T5= 4'b1100, T6= 4'b1101;
reg[3:0] Present_state= Default;

DataPath DUT(PCout, Zlowout, MDRout, MARin, Zin, PCin, MDRin, IRin, Yin, Read,
Write, Operator, clk, clear,
Gra, Grb, Grc, Rin, Rout, BAout, Cout, ConIn);

initial begin
    clk = 0;
    forever #10 clk = ~clk;
end

always @(posedge clk) //finite state machine; if clk rising-edge
begin
    case (Present_state)
        Default      :   #40 Present_state = T0;
        T0           :   #40 Present_state = T1;
        T1           :   #40 Present_state = T2;
        T2           :   #40 Present_state = T3;
        T3           :   #40 Present_state = T4;
        T4           :   #40 Present_state = T5;
        T5           :   #40 Present_state = T6;
    endcase
end

always @(Present_state) // do the required job in each state
begin
    case (Present_state) //assert the required signals in each
clk cycle
        Default: begin
            PCout <= 0;   Zlowout <= 0;   MDRout<= 0;   //initialize the
signals
            MARin <= 0;   Zin <= 0;
            PCin <=0;   MDRin <= 0;   IRin <= 0;   Yin <= 0;
            // incPC <= 0;

```

```

        Read <= 0;  Operator <= 5'b00000;
        Gra<= 0; Grb<= 0; Grc<= 0; Rin<= 0; Rout<= 0; BAout<= 0; Cout<=0;
        // clear <= 1; //initialize registers to 0
        // #10 clear <= 0;
    end

    T0: begin
        //load value in PC register (0) in MAR
        #5 PCout <= 1;
        #5 MARin <= 1;  //IncPC <= 1; Zin <= 1; used to inc PC by 4
        // incPC <= 1;
        // Zin <= 1;
    end

    T1: begin
        // Zlowout <= 1; PCin <= 1;
        PCout <= 0;
        //MDR will grab value from ram @ address 0, this address should
        contain instruction
        #5 Read <= 1; // Mdatain <= 1;
        #5 MDRin <= 1;
    end

    end

    T2: begin
        Read <= 0;
        MARin <= 0;
        MDRin <= 0;
        //load MDR value to bus which contains instruction, instruction
        is then stored in IR
        MDRout<= 1; IRin <= 1;
    end

    end

    T3: begin
        MDRout<= 0;
        IRin <= 0;

        Gra <= 1;
        Rout <= 1;
        ConIn <= 1;
        //set to 1 to generate R0out = 1 and store value of R0 (0) into Y
        register
        #5 Gra <= 0;
    end

    end

    T4: begin

```

```

        Rout <= 0;
        ConIn <= 0;

        PCout <= 1; Yin <= 1;
    end

T5: begin
        PCout <= 0; Yin <= 0;

        Cout <= 1;
        Operator <= 5'b00011; // ADD
        Zin <= 1;

        // store Z register contents (85) in bus
        // Zlowout <= 1;
        // load 85/busMuxOut into MAR to get address of 85
        // MARin <= 1;
    end


T6: begin
        Cout <= 0;
        Zin <= 0;

        Zlowout <= 1;
        // PC <= Con;
        // read from ram at address 85 and load that value in MDR -> we
will need to have a preset value in memory at address 85
        // Read <= 1;
        // MDRin <= 1;

    end


endcase
end
endmodule

```

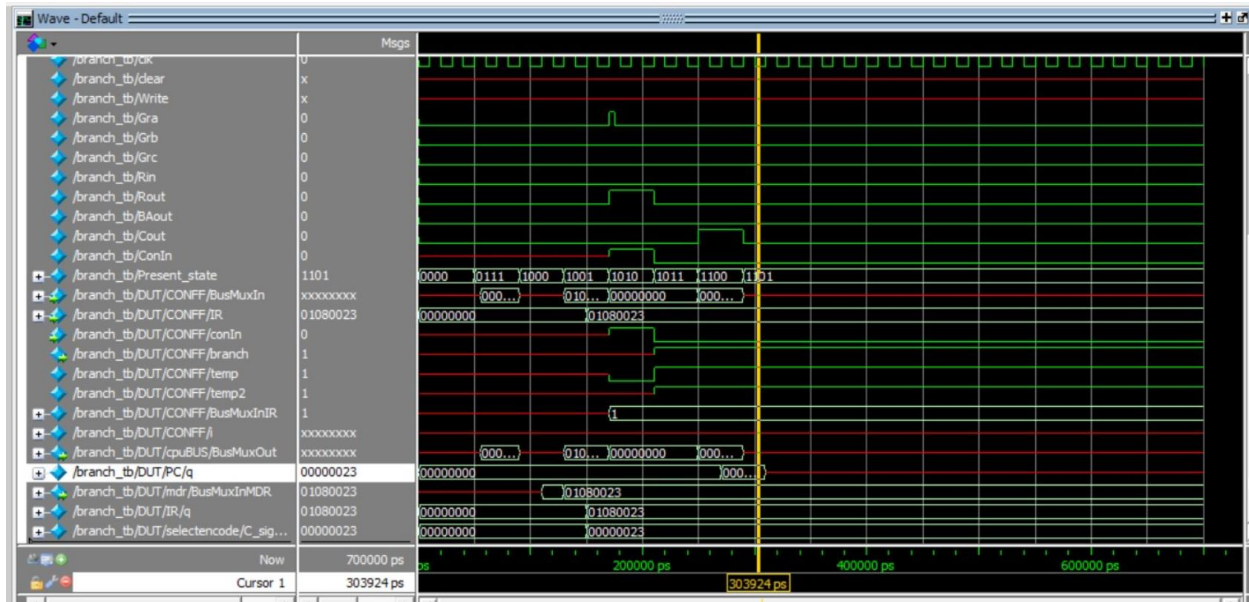

Brnz instruction – brnz R2, 35


This instruction shows that the design can perform a brnz branch (branch if non-zero) operation on 35 and the value of R2. The steps T0-T2 are executed first, performing the fetch instruction. Then, an operation is performed to determine whether or not to branch. If required, the branch is then performed. Refer to the brzr instruction for the testbench code. The same testbench was used for all branch operations, only the operation code was changed for each.

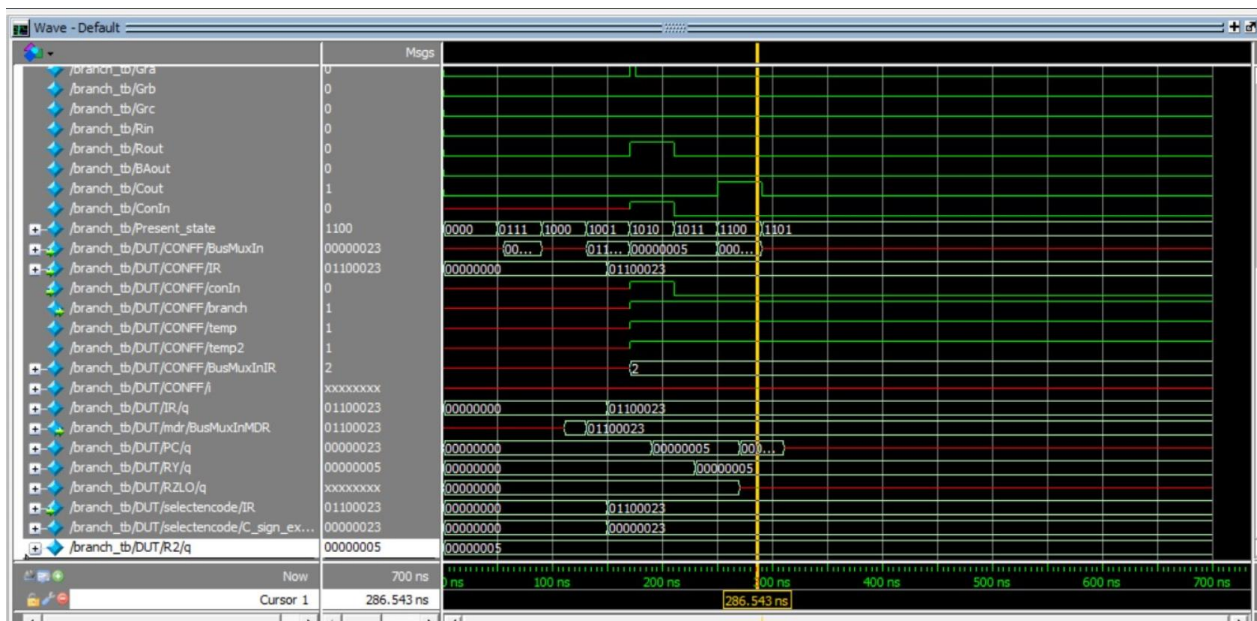

Brpl instruction – brpl R2, 35

This instruction shows that the design can perform a brpl branch (branch if positive) operation on 35 and the value of R2. The steps T0-T2 are executed first, performing the fetch instruction.

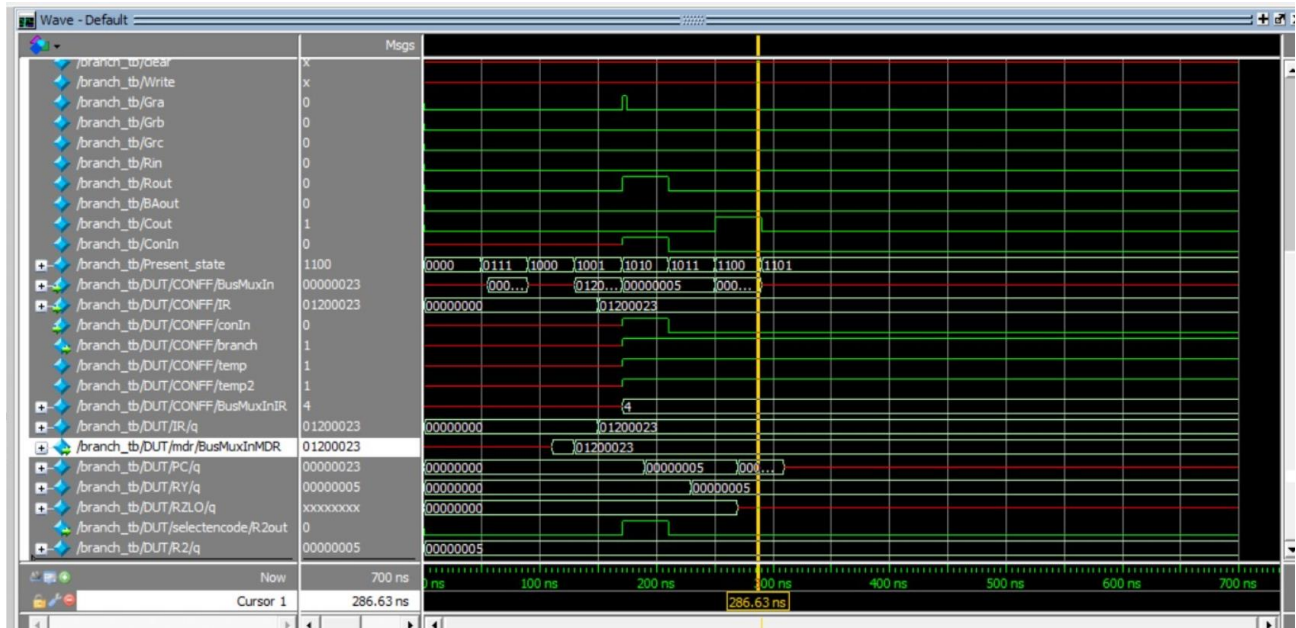Then, an operation is performed to determine whether or not to branch. If required, the branch is then performed. Refer to the brzr instruction for the testbench code. The same testbench was used for all branch operations, only the operation code was changed for each.



Brmi instruction – brmi R2, 35

This instruction shows that the design can perform a brmi branch (branch if negative) operation on 35 and the value of R2. The steps T0-T2 are executed first, performing the fetch instruction. Then, an operation is performed to determine whether or not to branch. If required, the branch is then performed. Refer to the brzr instruction for the testbench code. The same testbench was used for all branch operations, only the operation code was changed for each.

